

Roll No. _____

[Total No. of Pages : 3

SIIS 69 A-2K12
B.Sc. IInd Semester Degree Examination
Electronics
Electronic Circuits
Paper - 2.3

Time : 3 Hours

Maximum Marks : 80

Instructions to Candidates:

- 1) Answer **all** the questions from **section - A**
- 2) Answer any **five** questions from **section - B**
- 3) Answer any **four** questions from **Section - C**.

Section - A

1. Choose the correct answer. (5×1=5)
- i) The current ICBO flows in
 - a) The emitter, base and collector leads.
 - b) The emitter and base leads
 - c) The emitter and collector leads
 - d) The collector and base leads.
 - ii) The operation of a JFET involves.
 - a) A flow of minority carriers.
 - b) A flow of majority carriers.
 - c) Recombination.
 - d) Negative resistance.
 - iii) If V_m is the peak voltage across the secondary of the transformer in a half - wave rectifier then the maximum voltage on the reverse biased diode is
 - a) V_m
 - b) $2V_m$
 - c) $\frac{V_m}{2}$
 - d) None.

- iv) Which of the following voltage regulator is preferred for providing. Large values of Load current.
- Zener diode shunt regulator.
 - Transistor series regulator.
 - Transistor shunt regulator.
 - None.
- v) The dc load line of a transistor circuit.
- Is a graph between I_C and V_{CE}
 - Is a graph between I_C and I_B
 - Is a graph between I_B and I_{BE}
 - None.

2. Fill in the blanks. (5×1=5)

- The collector current is 100 mA. If the current gain is 100, the base current is ____.
- An improperly - biased transistor produces _____ in the output signal.
- The overall voltage gain of a cascaded amplifier is equal to the ____ of the gains of individual stages.
- The conduction angle of class- B amplifiers is _____ degrees.
- Push-Pull operation requires two transistors of the same type with ____ characteristics.

3. State whether following statements are TRUE or FALSE. (5×1=5)

- In an NPN transistor, collector is positive with respect to base.
- FETs have high input impedance and low output impedance.
- Ripple factor of a full wave rectifier is about half the value of a half wave rectifier.
- The purpose of biasing a circuit is to establish a proper stable dc operating point.
- The chief merit of RC coupling is that it is inexpensive.

Section - B

Answer any five (5×5=25)


- Explain the working PNP transistor.
- Write the difference between BJT and FET.
- With a neat circuit diagram explain PIV for Centre-tap FW rectifier.
- What are h -parameters? Draw the hybrid equivalent circuit of a transistor in CE mode.
- Define thermal runaway? Explain the reasons for thermal runaway.
- Briefly explain the difference between voltage and power amplifiers.
- Why more than one stage of amplifiers need in practical circuits. What are the different coupling schemes

Section - C

Answer any four

(4×10=10)

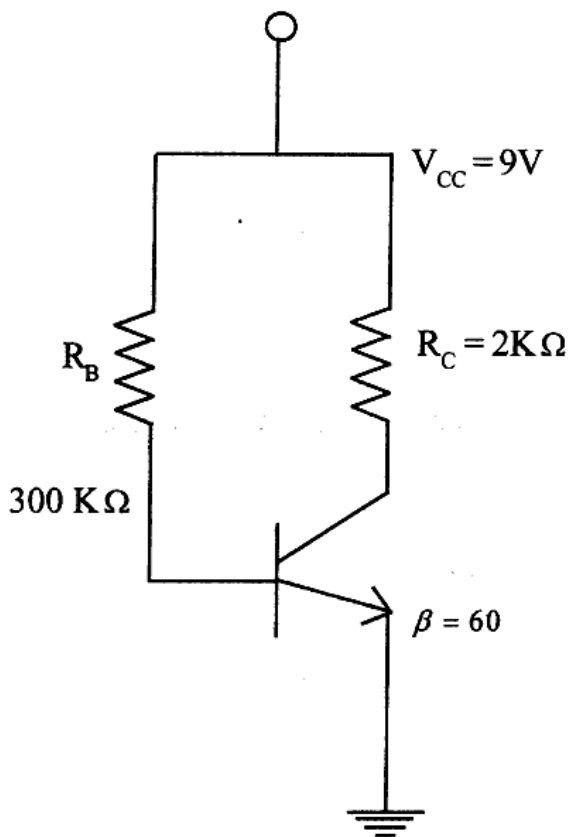11. With a neat circuit diagram explain the input and output characteristics of common emitter configuration.
12. a) Explain construction and I-V characteristics of UJT.
b) Derive the relation between FET Parameters. (6+4)
13. a) With a neat circuit diagram explain bridge rectifier.
b) Show that ripple factor of full wave rectifier is 0.48. (6+4)
14. a) Explain fixed bias circuit without emitter resistor. What are its advantages.
b) Determine the values of I_B , I_C and V_{CE} for the given circuit. (6+4)



15. With a neat Circuit diagram explain the frequency response of two stage RC Coupled amplifier.
16. With a neat circuit diagram explain transformer coupled class-B push Pull amplifier. Derive an expression for its power efficiency.