

Roll No. \_\_\_\_\_

No. of Pages : 3

**SVIS-N-303-A-18**

**B.Sc. IV<sup>th</sup> Semester Degree Examination**

**PHYSICS**

**(Electronics, Astrophysics, Plasma and Diagnostic Physics)**

**paper-6.2**

**(New)**

Time : 3 Hours

Maximum Marks : 80

**Instructions to candidates:**

- i. Answer **all** the questions from **Section-A**
- ii. Answer **any five** from **Section-B**
- iii. Answer **any four** from **Section-C**

**Section-A**

**I. Answer the following questions in one or two sentences**

**(15×1 = 15)**

- 1) State Thevenine theorem
- 2) Why, Zener diode is heavily doped
- 3) What is tunnel diode
- 4) What is the significance of arrow in the transistor symbol
- 5) Mention any two advantages of SCR as a switch
- 6) What is an Integrated Circuits
- 7) What is D.C load line
- 8) Mention any two advantages of Oscillator
- 9) What is undamped Oscillation
- 10) What is satellite communication
- 11) Give the circuit symbol of X-OR gate
- 12) What is Black hole? Who discovered it
- 13) What is transport phenomena
- 14) What is the normal range of blood pressure
- 15) What can C.T scans shows

**Section-B**

**II. Answer any Five Questions**

(5 × 5 = 25)


- 16) State and explain Norton's theorem
- 17) Draw and explain IV-Characteristic of PN-junction diode
- 18) What is light emitting diode(LED)? Explain the theory of LED
- 19) Discuss the Frequency modulation(FM) and mention their advantages
- 20) What is decimal and binary system? Explain the conversion of binary to decimal with example
- 21) Explain chandrashekar mass limit.
- 22) Explain briefly Inelastic collision in plasma

**Section-C**

**III. Answer any Four Questions**

(4 × 10 = 40)

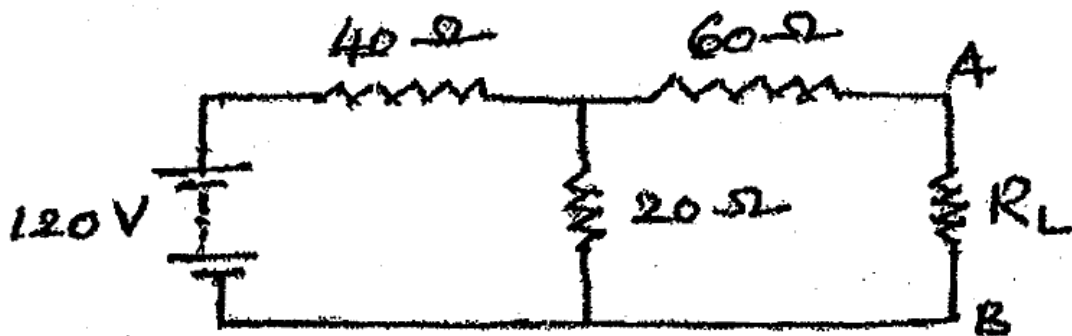- 23) a) State Maximum power transfer theorem. (1+5+4)
- b) Derive the condition for transfer of maximum power from a source to a load
- c) Calculate the value of load resistance  $R_L$  to which maximum power may be transferred from the circuit show in fig(1). Also find the maximum power



- 24) a) What is transistor? Draw and explain the characteristic of NPN-transistor in CB and CE mode.
- b) For the circuit of a Zener diode the input voltage  $E_i = 120V$ , series resistance  $R_s = 5K\Omega$ , zener voltage  $V_Z = 50V$  and load resistance  $R_L = 10k\Omega$ . Find the current flowing through zener diode (7+3)
- 25) a) What is an operational amplifier? Explain how an operational amplifier can be used as an Inverting amplifier

- b) Explain the construction and working of a Wein bridge Oscillator
  - c) The frequency of a Wein bridge oscillator is 4 KHz. the value of the capacitor in the bridge network is 300pf. Find the value of the resistor. (4+4+2)
- 26) a) What is demodulation? What are essentials is demodulation?
- b) A carrier wave of 500 watts is subjected to 100% amplitude modulation. Determine
- i) Power in sidebands and
  - ii) Power of modulated wave
- c) How is a NAND-gate formed? Explain (3+3+4)
- 27) a) Explain the physical properties of stars
- b) What is recombination? Explain
- 28) a) Describe the palpatory method to measure diastolic and systolic blood pressure
- b) Write a note on Radiation measurement. (5+5)
-