

6422 – A11 – IS BSc (CS) – N – 19

FIRST SEMESTER B.Sc. (CS) DEGREE EXAMINATION, NOVEMBER 2019
BASIC ELECTRICALS AND ELECTRONICS

Time : 3 Hours]

[Max. Marks : 80

Answer any five full questions.

Scientific calculators are allowed.

- a) Define Alternating Current and derive the expression for Alternating Current.
i.e, $i = I_m \sin \omega t$.
- b) Define Average value of alternating voltage and show that $I_{avg} = 0.637 I_m$.
- c) Find the relationship between
- 1) Time period and frequency
 - 2) Angular velocity and frequency. 6 + 6 + 4
- a) Explain RLC series circuit with the help of a neat circuit diagram and phasor diagram and derive expression for impedance (Z) and phase angle (ϕ).
- b) A capacitor of capacitance $100\mu F$ is connected in series with the resistor of resistance 100Ω across 230V, 50HZ supply. Find the
- 1) Impedance (Z)
 - 2) Total current (I)
 - 3) Power factor ($\cos \phi$).
- c) Explain the different ways of connecting 3-phases and explain elementary 3-phase alternator with necessary equations. 6 + 4 + 6
- a) Explain the construction and principle of operation of transformer with necessary equations.
- b) Write a note on losses in transformer.
- c) Write the emf equation of transformer. 8 + 6 + 2
- a) Explain why PN-Junction diode allows flow of current in only one direction and Zener diode allows flow of current in both the directions.
- b) Why to use filters in Rectifier circuits? Draw the circuit diagram of center tap Rectifier with filter.
- c) Draw the circuit diagrams for Zener diode in forward bias and reverse bias conditions. 6 + 6 + 4


[P.T.O.]

5. a) With necessary circuit diagram explain the CE configuration along with I/P and O/P characteristics of NPN transistor.

- b) With neat circuit diagram explain the working of RC-coupled amplifier.

8 +

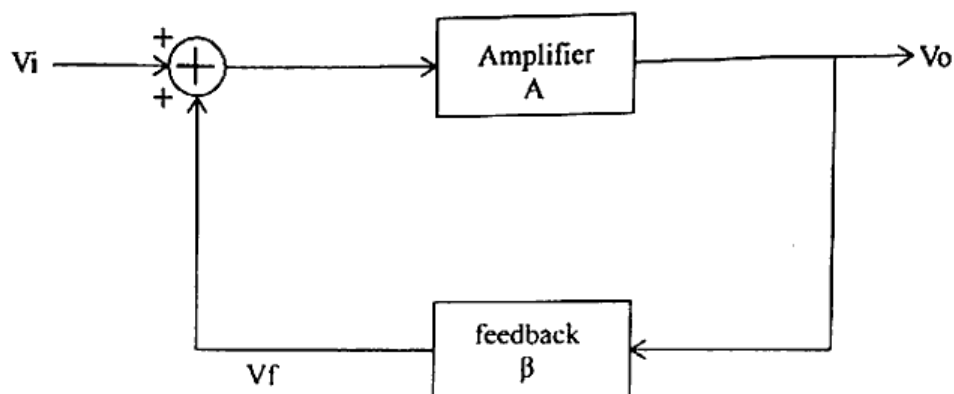6. a) Define oscillator and show that overall gain of the following oscillator is $\frac{A}{1 - A\beta}$



- b) With a neat circuit diagram explain the working of Hartley oscillator. Also specify the expression for output frequency.

- c) Explain Ideal characteristics of OPAMP.

4 + 6 +

7. a) With necessary equations and circuit diagram explain how OPAMP can be used as adder or summing amplifier.

- b) Define Amplitude modulation and obtain the expression for amplitude modulated wave.

- c) Write a note on Interferometer.

6 + 6 +

8. Write short notes on any four of the following:

- a) LCR Bridge

- b) Block diagram of communication system

- c) IC-741

- d) Depletion Region

- e) Addition of Alternating quantities.

4 + 4 + 4 +