

**3230 – C81 – IISS – N – 14**

**THIRD SEMESTER B.Sc. DEGREE EXAMINATION, NOVEMBER 2014**

**ELECTRONICS**

**(New Syllabus)**

**Time : 3 Hours]**

**[Max. Marks : 80**

*Answer all questions in the same answer book.*

**PART – A (Marks:  $10 \times 2 = 20$ )**

*Answer any ten of the following.*

1. What is Optoelectronics?
2. Mention the applications of solar cell.
3. Convert  $(DAD)_{16}$  into Decimal member.
4. Find the difference between 1100 and 1001 using 1's compliment.
5. What is ASCII code? Give any two examples?
6. Draw the logic circuit for  $\overline{AB} + B + C$
7. Prove that  $(A+B)(A+C) = A+BC$  using Boolean algebra.
8. Define rise time and fall time in a pulse.
9. What is decoder?
10. Draw a circuit diagram of Half subtractor.
11. What is shift register? Give examples.
12. Write the difference between synchronous and asynchronous counters.

**PART – B (Marks:  $6 \times 5 = 30$ )**

*Answer any six of the following.*

13. Explain the working of photodiode and draw the VI-Characteristics.
14. Discuss the conversion of binary to decimal and vice versa, with example.
15. Write a note on BCD-code.
16. A four variable truth table has low output from 0000 to 1000 and high output for 1001, don't care for 1010 to 1111. Write the simplified boolean equation using k-map.
17. Explain with circuit CMOS inverter.
18. What is a full adder? Draw its circuit diagram and truth table.
19. Explain with circuit diagram, working of 3 bit D to A converter using binary weighted resistor.
20. What is flip-flop? Explain D-Flip-flop.

**[P.T.O.]**

**PART – C (Marks:  $3 \times 10 = 30$ )***Answer the following.*

21. Describe construction, working and applications of photoconductive cell.

Or

Explain the conversion of grey to binary and vice-versa using XOR-gate with one illustrative example.

22. Name the universal gates. Why they are called So? Verify their universal property.

Or

Describe 4:1 multiplexer and 1:4 demultiplexer using gates.

23. Explain clocked JK-flip-flop using gates, discuss race around condition.

Or

With a circuit diagram and timing diagram explain the working of decade counter.